

- (b) Find transfer function  $\frac{I_2}{V_1}$  for the Network shown in Fig. 10(b). 7

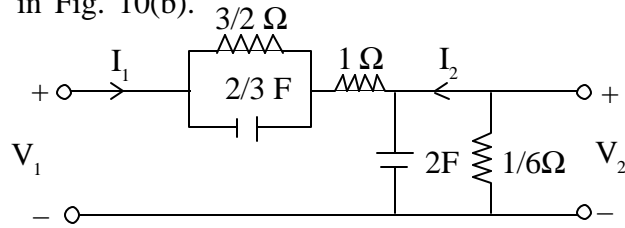


Fig. 10(b)

11. (a) Define ABCD parameters and derive the condition for reciprocity in terms of ABCD parameters. 7  
 (b) Find the Z-parameter of the Network shown in Fig. 11(b). 7

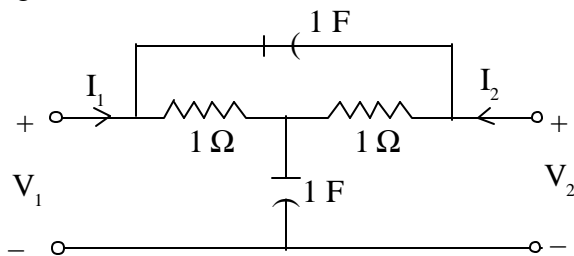


Fig. 11(b)

OR

12. (a) Compare series and parallel resonant circuit. 6  
 (b) A 400 V, 3 phase supply feeds an unbalanced three wire star-connected load. The branch impedances of the load are  $Z_R = (4 + j8)\Omega$ .  $Z_Y = (3 + j4)\Omega$  and  $Z_B = (15 + j20)\Omega$ . Find the line current and voltage across each phase impedance. Assume RBY as phase sequence. 8

**Faculty of Engineering & Technology**  
**Third Semester B.E. (Electrical Engg.)**  
**(C.B.S.) Examination**  
**NETWORK ANALYSIS**

Time : Three Hours] [Maximum Marks : 80

**INSTRUCTIONS TO CANDIDATES**

- (1) All questions carry marks as indicated.
  - (2) Due credit will be given to neatness and adequate dimensions.
  - (3) Assume suitable data wherever necessary.
  - (4) Illustrate your answers wherever necessary with the help of neat sketches.
  - (5) Use of non-programmable calculator is permitted.
1. (a) Using source transformation, convert the ckt. shown in Fig. 1(a) into single voltage source and single resistance. 6


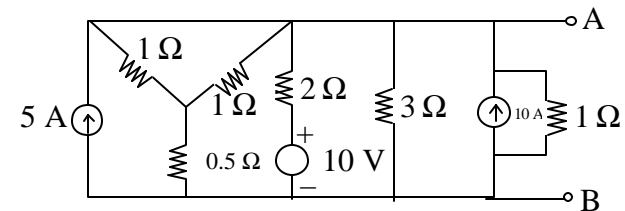



Fig. 1(a)

- (b) Determine the Mesh current  $I_1$ ,  $I_2$  and  $I_3$  in the Network of Fig. 1(b). 7

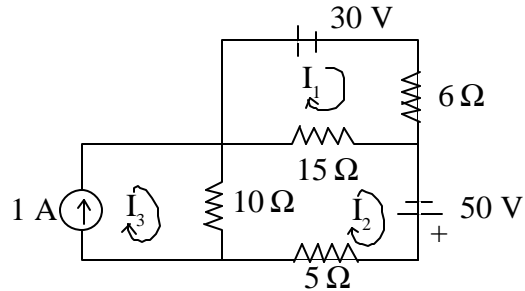


**Fig. 1(b)**  
**OR**

2. (a) Determine the magnitude of voltage source  $V_1(t)$  which results of 20 volt across  $5 \Omega$  resistance as shown in Fig. 2(a). 7

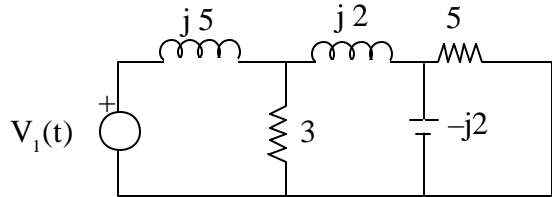


**Fig. 2(a)**

- (b) For the Network shown in Fig. 2(b), write Mesh equations in matrix form. 6

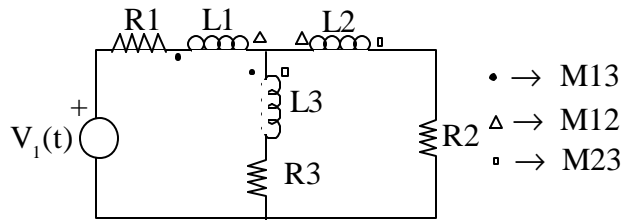


**Fig. 2(b)**

3. (a) Find the voltage  $V$ , which makes the current in  $10 \Omega$  resistance is zero using nodal analysis. 6

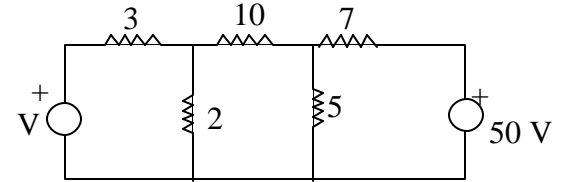

**Fig. 3(a)**


- (b) Write the matrix form of the nodal equation for the Network shown. 7

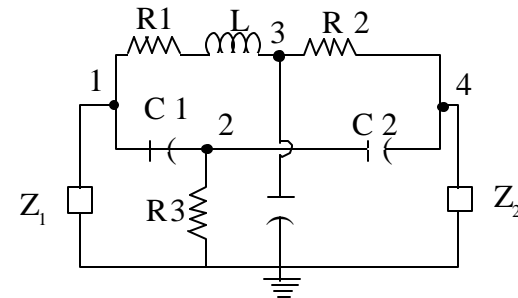

**Fig. 3(b)**


**OR**

4. (a) Define Dual Network. Draw the dual of the following Network. Write the condition satisfied by Dual Network. 6

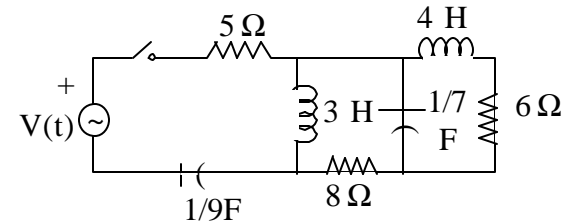


**Fig. 4(a)**

- (b) Using nodal analysis for the 'Fig. 4(b)', find the power factor of source  $V_A$  and  $V_B$ . 7

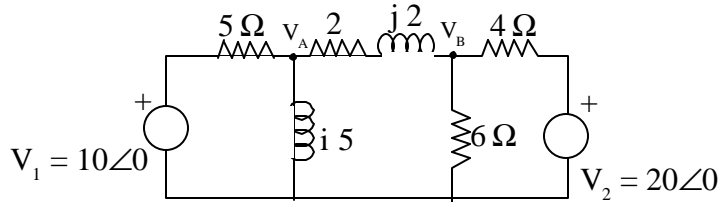


**Fig. 4(b)**

5. (a) In the Network of Fig 5(a) shown below; determine  $V_b$  by principle of Superposition. 7

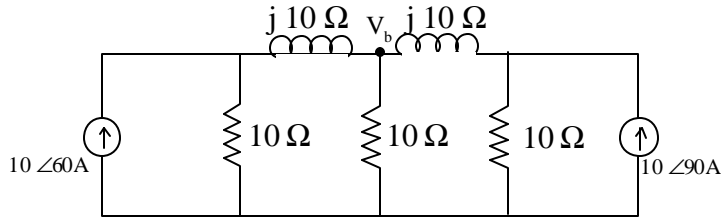

**Fig. 5(a)**


- (b) Find out the current flowing through branch AB of Network shown in Fig. 5(b) by applying Norton's theorem and hence find Thevenin's equivalent network. 7

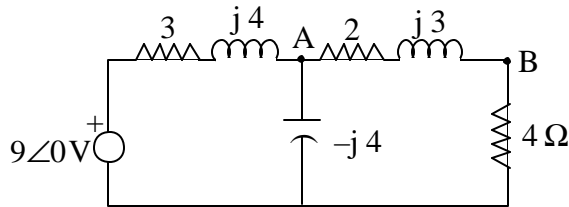

**Fig. 5(b)**


**OR**

6. (a) Find the current I and verify the reciprocity theorem for the Network shown in Fig. 6(a). 7

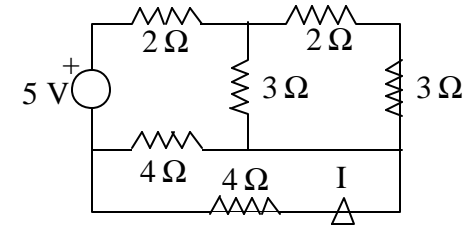


**Fig. 6(a)**

- (b) For the Network shown in Fig. 6(b) the 5 Ω resistor is changed to 8 Ω. Determine the resulting change in current  $\Delta I$  through  $(3+j4)\Omega$  impedance branch using Compensation theorem. 7

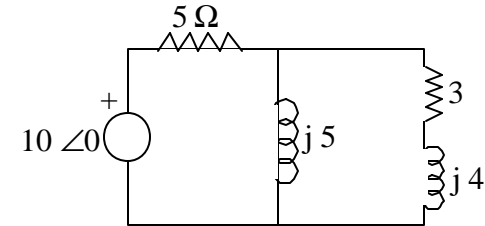

**Fig. 6(b)**

7. (a) In the Network of Fig. 7(a), the switch is opened at  $t = 0$ , find  $i_2(t)$ . 7

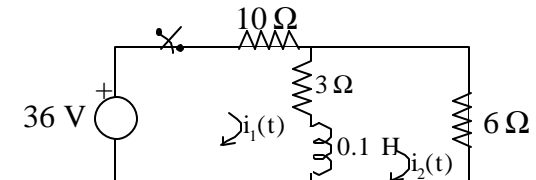

**Fig. 7(a)**


- (b) Derive the expression for the impulse response of series RC Network using Laplace transform.

6

**OR**

8. (a) In the Network of Fig. 8(a) was initially in the steady state with the switch in the position a. At  $t = 0$  the switch goes from a to b. find expression for voltage  $V(t)$  for  $t > 0$ .


7

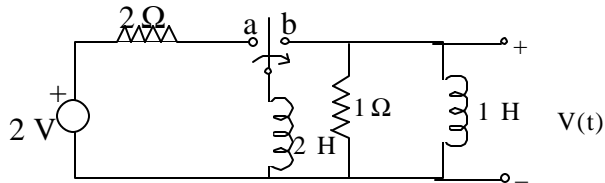

**Fig. 8(a)**

- (b) Find the Laplace transform of the waveform shown in Fig 8(b).


6

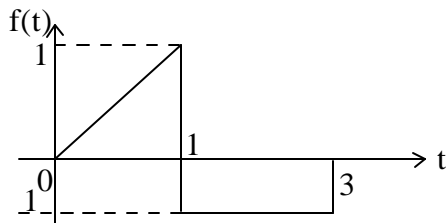

**Fig. 8(b)**

9. (a) Find the driving point admittance function of the Network shown.

4

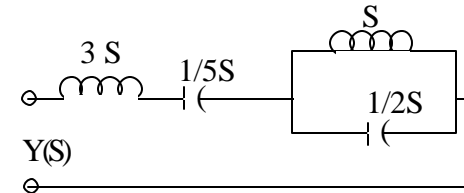

**Fig. 9(a)**

- (b) Define the following terms :

(1) Driving point function

(2) Transfer function

(3) Current gain.

3

- (c) The voltage  $V(s)$  of a Network is given by

$$V(s) = \frac{3s}{(s+2)(s^2+2s+2)}$$


Plot its pole-zero diagram and hence obtain  $V(t)$  from pole-zero diagram.

6

**OR**

10. (a) Determine the voltage transfer function  $\frac{V_2}{V_1}$  for the Network shown in Fig. 10(a).

6

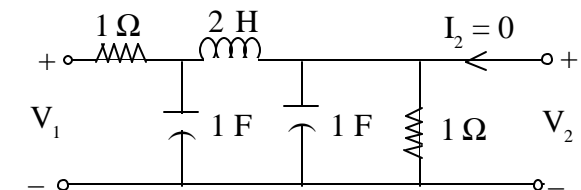

**Fig. 10(a)**