

Mesh Analysis


Mesh Analysis

- Mesh analysis applies KVL to find unknown currents.
- A mesh is a loop that does not contain any other loops.
- The current through a mesh is known as the mesh current.
- Assume for simplicity that the circuit contains only voltage sources.

Mesh Analysis Steps

1. Assume mesh currents $i_1, i_2, i_3, \dots, i_l$, to the l meshes.
2. Apply KVL to each of the l meshes and use Ohm's law to express the voltages in terms of the mesh currents.
3. Solve the l resulting simultaneous equations to find the mesh currents or form a matrix equation using mesh equations.
4. Find the individual parameters by solving Mesh equations.

Example

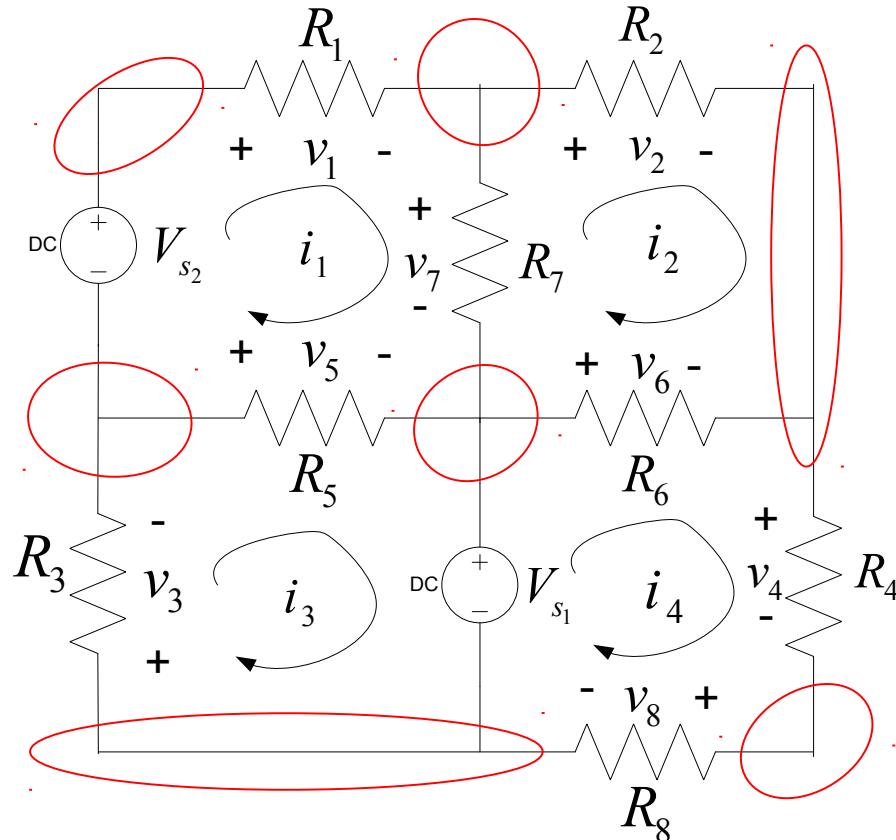


Number of nodes, $n = 7$

Number of loops, $l = 4$

Number of branches, $b = 10$

Example

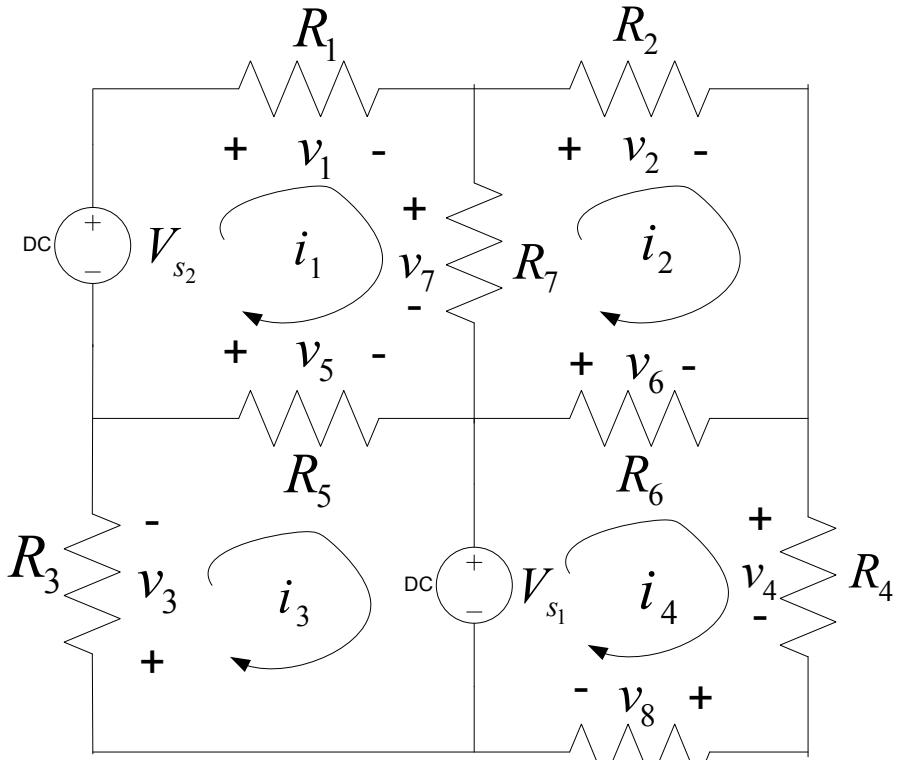

Apply KVL to each mesh

$$\text{Mesh 1: } -V_{s_2} + v_1 + v_7 - v_5 = 0$$

$$\text{Mesh 2: } v_2 - v_6 - v_7 = 0$$

$$\text{Mesh 3: } v_5 + V_{s_1} + v_3 = 0$$

$$\text{Mesh 4: } v_4 + v_8 - V_{s_1} + v_6 = 0$$

$$\text{Mesh 1: } -V_{s_2} + v_1 + v_7 - v_5 = 0$$

$$\text{Mesh 2: } v_2 - v_6 - v_7 = 0$$

$$\text{Mesh 3: } v_5 + v_{s_1} + v_3 = 0$$

$$\text{Mesh 4: } v_4 + v_8 - V_{s_1} + v_6 = 0$$


Express the voltage in terms of the mesh currents:

$$\text{Mesh 1: } -V_{s_2} + i_1 R_1 + (i_1 - i_2) R_7 + (i_1 - i_3) R_5 = 0$$

$$\text{Mesh 2: } i_2 R_2 + (i_2 - i_4) R_6 + (i_2 - i_1) R_7 = 0$$

$$\text{Mesh 3: } (i_3 - i_1) R_5 + V_{s_1} + i_3 R_3 = 0$$
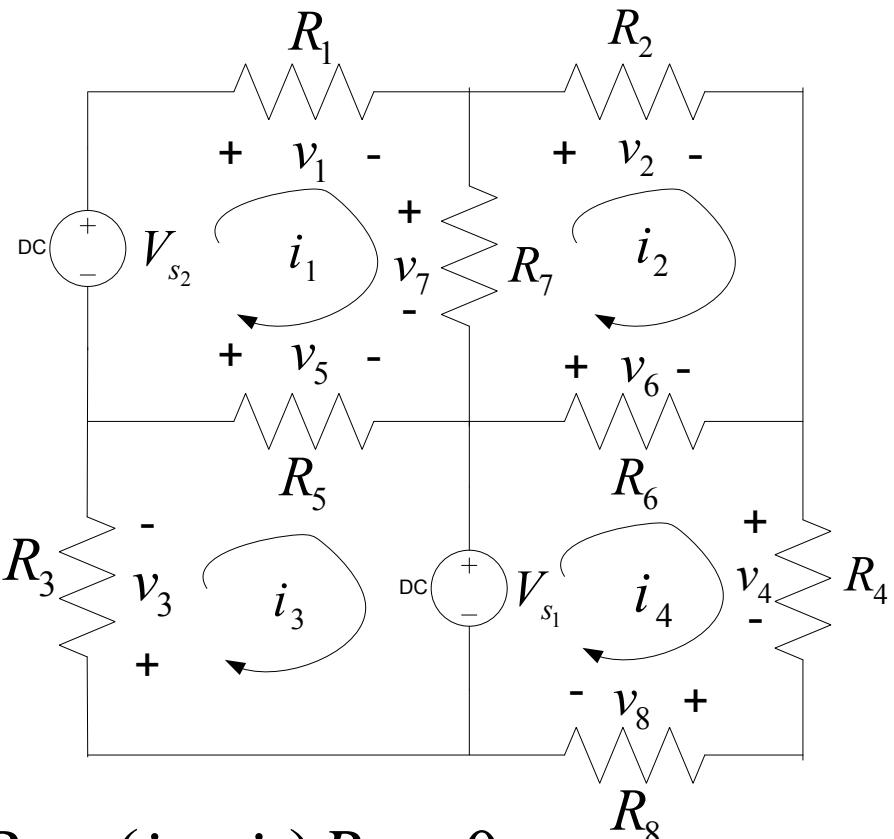
$$\text{Mesh 4: } i_4 R_4 + i_4 R_8 - V_{s_1} + (i_4 - i_2) R_6 = 0$$



$$\text{Mesh 1: } -V_{s_2} + i_1 R_1 + (i_1 - i_2) R_7 + (i_1 - i_3) R_5 = 0$$

$$\text{Mesh 2: } i_2 R_2 + (i_2 - i_4) R_6 + (i_2 - i_1) R_7 = 0$$

$$\text{Mesh 3: } (i_3 - i_1) R_5 + V_{s_1} + i_3 R_3 = 0$$

$$\text{Mesh 4: } i_4 R_4 + i_4 R_8 - V_{s_1} + (i_4 - i_2) R_6 = 0$$

$$\text{Mesh 1: } (R_1 + R_5 + R_7) i_1 - R_7 i_2 - R_5 i_3 = V_{s_2}$$

$$\text{Mesh 2: } -R_7 i_1 + (R_2 + R_6 + R_7) i_2 - R_6 i_4 = 0$$

$$\text{Mesh 3: } -R_5 i_1 + (R_3 + R_5) i_3 = -V_{s_1}$$

$$\text{Mesh 4: } -R_6 i_2 + (R_4 + R_6 + R_8) i_4 = V_{s_1}$$

$$\text{Mesh 1: } (R_1 + R_5 + R_7)i_1 - R_7i_2 - R_5i_3 = V_{s_2}$$

$$\text{Mesh 2: } -R_7i_1 + (R_2 + R_6 + R_7)i_2 - R_6i_4 = 0$$

$$\text{Mesh 3: } -R_5i_1 + (R_3 + R_5)i_3 = -V_{s_1}$$

$$\text{Mesh 4: } -R_6i_2 + (R_4 + R_6 + R_8)i_4 = V_{s_1}$$

$$\begin{pmatrix} R_1 + R_5 + R_7 & -R_7 & -R_5 & 0 \\ -R_7 & R_2 + R_6 + R_7 & 0 & -R_6 \\ -R_5 & 0 & R_3 + R_5 & 0 \\ 0 & -R_6 & 0 & R_4 + R_6 + R_8 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{pmatrix} = \begin{pmatrix} V_{s_2} \\ 0 \\ -V_{s_1} \\ V_{s_1} \end{pmatrix}$$

$$\begin{pmatrix} R_1 + R_5 + R_7 & -R_7 & -R_5 & 0 \\ -R_7 & R_2 + R_6 + R_7 & 0 & -R_6 \\ -R_5 & 0 & R_3 + R_5 & 0 \\ 0 & -R_6 & 0 & R_4 + R_6 + R_8 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{pmatrix} = \begin{pmatrix} V_{s_2} \\ 0 \\ -V_{s_1} \\ V_{s_1} \end{pmatrix}$$


$$\mathbf{R}\mathbf{i} = \mathbf{v}$$

R is an $l \times l$ *symmetric* resistance matrix

i is a $1 \times l$ vector of mesh currents

V is a vector of voltages representing “known” voltages

Writing the Mesh Equations by Inspection

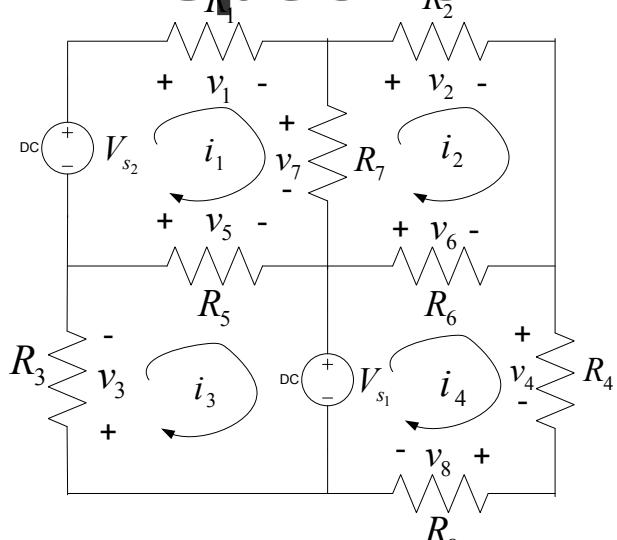

$$\begin{pmatrix} R_1 + R_5 + R_7 & -R_7 & -R_5 & 0 \\ -R_7 & R_2 + R_6 + R_7 & 0 & -R_6 \\ -R_5 & 0 & R_3 + R_5 & 0 \\ 0 & -R_6 & 0 & R_4 + R_6 + R_8 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{pmatrix} = \begin{pmatrix} V_{s_2} \\ 0 \\ -V_{s_1} \\ V_{s_1} \end{pmatrix}$$

- The matrix \mathbf{R} is symmetric, $r_{kj} = r_{jk}$ and all of the off-diagonal terms are negative or zero.

The r_{kk} terms are the sum of all resistances in mesh k .

The r_{kj} terms are the negative sum of the resistances common to BOTH mesh k and mesh j .

The v_k (the k^{th} component of the vector \mathbf{v}) = the algebraic sum of the independent voltages in mesh k , with voltage rises taken as positive


MATLAB Solution of Mesh Equations

$$\begin{pmatrix} R_1 + R_5 + R_7 & -R_7 & -R_5 & 0 \\ -R_7 & R_2 + R_6 + R_7 & 0 & -R_6 \\ -R_5 & 0 & R_3 + R_5 & 0 \\ 0 & -R_6 & 0 & R_4 + R_6 + R_8 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{pmatrix} = \begin{pmatrix} V_{s_2} \\ 0 \\ -V_{s_1} \\ V_{s_1} \end{pmatrix}$$

$$\mathbf{R}\mathbf{i} = \mathbf{v}$$

$$\mathbf{i} = \mathbf{R}^{-1} \mathbf{v}$$

Test with numbers

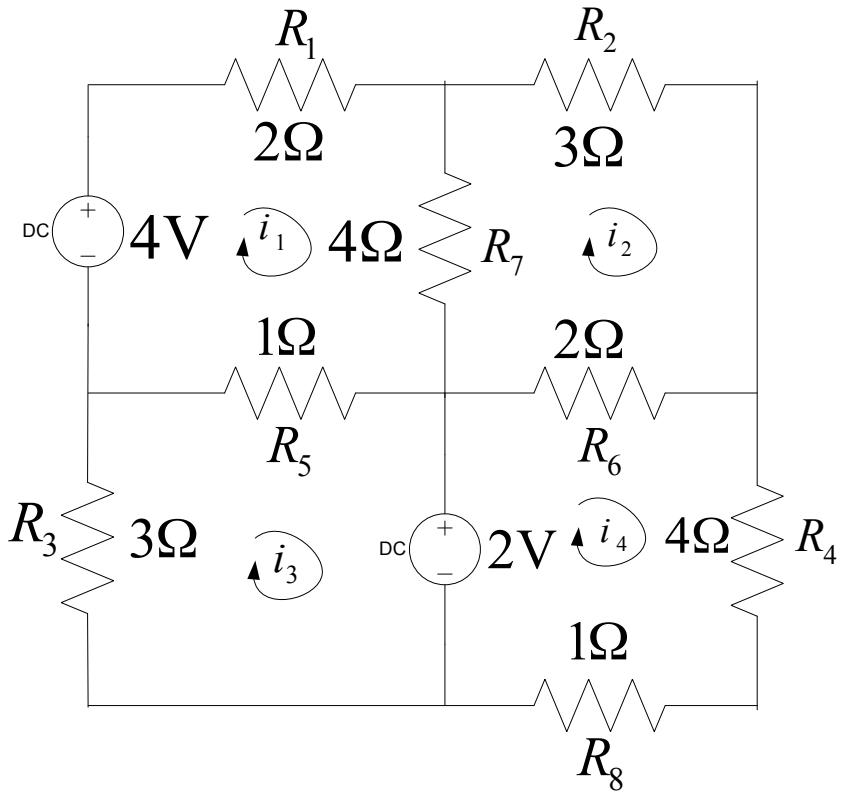

$$\begin{pmatrix} 2+4+1 & -4 & -1 & 0 \\ -4 & 3+2+4 & 0 & -2 \\ -1 & 0 & 3+1 & 0 \\ 0 & -2 & 0 & 2+4+1 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{pmatrix} = \begin{pmatrix} 4 \\ 0 \\ -2 \\ 2 \end{pmatrix}$$

Test with numbers

$$\begin{pmatrix} 2+4+1 & -4 & -1 & 0 \\ -4 & 3+2+4 & 0 & -2 \\ -1 & 0 & 3+1 & 0 \\ 0 & -2 & 0 & 2+4+1 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{pmatrix} = \begin{pmatrix} 4 \\ 0 \\ -2 \\ 2 \end{pmatrix}$$

$$\begin{pmatrix} 7 & -4 & -1 & 0 \\ -4 & 9 & 0 & -2 \\ -1 & 0 & 4 & 0 \\ 0 & -2 & 0 & 7 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{pmatrix} = \begin{pmatrix} 4 \\ 0 \\ -2 \\ 2 \end{pmatrix}$$

$$\mathbf{R}\mathbf{i} = \mathbf{v}$$